




SCIENCE CH: 9 ELECTRICITY AND CIRCUITS

Class VI

I. **Choose the correct answer:**

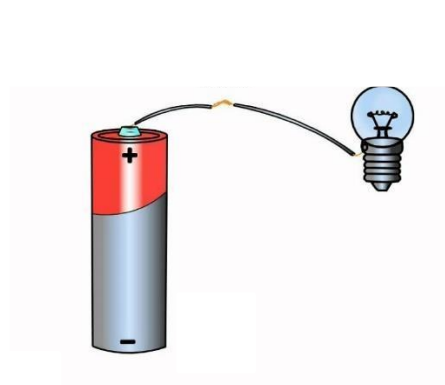1. An electric cell is a device which converts chemical energy into
 - a. Heat energy
 - b. light energy
 - c. electrical energy
2. The filament of an electric bulb is made up of
 - a. Iron metal
 - b. Tungsten
 - c. Aluminium
3. The circuit is said to be closed when the switch is in
 - a. OFF position
 - b. ON position
4. Identify the fault in the connection shown below:



- a. The circuit is closed.
 - b. The terminals of the cell are not connected properly to the terminals of the bulb.
 - c. The switch is in the 'OFF' position.
5. Copper wires used as connecting wires in the electric circuits are covered by plastic coating. Why?




- a. Plastic is an insulator which does not allow electricity to pass through it.
- b. Plastic coating prevents accidental contact with conducting wires.
- c. All of these

II. **Draw a circuit diagram to represent the electric circuit shown below:**



6.

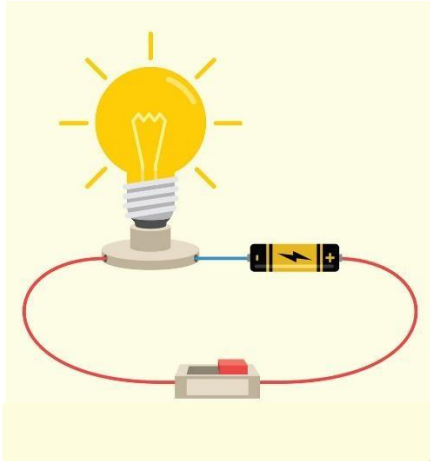

III. Answer the following questions:

7. Name some objects which use electricity for their working.
8. Define conductors and insulators. Give one example of each.
9. What will happen if you join the two terminals of a cell without connecting them through a bulb or switch?



10. Examine the picture shown below carefully and answer the following questions:



- i. The bulb is not glowing even after all the connections are made. Why?
- ii. What changes can be made in the circuit to make the bulb glow?